

# **FINAL EXAM**

**EE315 Spring 2017—Dr. B**


**NAME** SOLUTION KEY

**DO ALL YOUR WORK ON THIS EXAM.  
USE THE BACK SIDES of EXAM PAPER IF  
NECESSARY BUT POINT ME WHERE YOU  
DID THAT.**

- **Your Equation “Cheat Sheet” must be turned in with the Exam.**
- **NO Cell PHONE Calculators allowed. Other calculators ok.**
- **Closed books/closed lecture notes.**
- **Each Problem worth 10 points.**

Why then, can one desire too much of a good thing? WILLIAM SHAKESPEARE, *As You Like It*

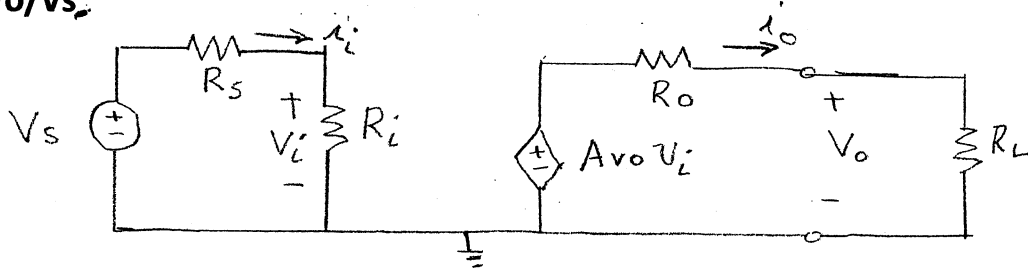**Problem 1:** For the circuit model of voltage amplifier below,  $A_{vo} = 100$  volts/volt when  $R_i = 10R_s$  and  $R_L = 10R_o$ . Compute the OVERALL VOLTAGE GAIN  $V_o/V_s$ .



$$V_i = \left( \frac{R_i}{R_i + R_s} \right) V_s = \left( \frac{10R_s}{11R_s} \right) V_s = \frac{10}{11} V_s$$

$$V_o = \left( \frac{R_L}{R_o + R_L} \right) 100 V_i = \left( \frac{10R_o}{11R_o} \right) 100 V_i$$

SOURCE  
p. 26 Textbook

$$V_o = \left( \frac{10}{11} \right) 100 V_i = \frac{10}{11} (100) \left( \frac{10}{11} \right) V_s$$

$$\frac{V_o}{V_s} = \frac{(100)(100)}{(11)(11)} = \boxed{82.64 \text{ volt/volt}}$$

2. Find the complex impedance at 10 K hertz for: ( nano is  $10^{-9}$  power, pico is  $10^{-12}$  power. Leave answer in form of  $Z = \text{real part} + \text{imaginary part}$ .

(a) a 1 K ohm resistor in series with a 10 nano-farad capacitor.

(b) a 10 K ohm resistor in series with a 100 millihenry inductor.


$$\begin{aligned} \text{(a)} \quad Z &= 1000 - \frac{j}{\omega C} = 1000 - \frac{j}{2\pi(10 \times 10^3)(10 \times 10^{-9})} \\ &= 1000 - \frac{j}{6.2832 \times 10^{-4}} \end{aligned}$$

$$Z = 1000 - j1591.54 \, \Omega$$

$$\text{(b)} \quad Z = 1000 + j(2\pi)(100 \times 10^{-3}) = 1000 + j.6283 \, \Omega$$

$$Z = 10000 + j.6283 \, \Omega$$

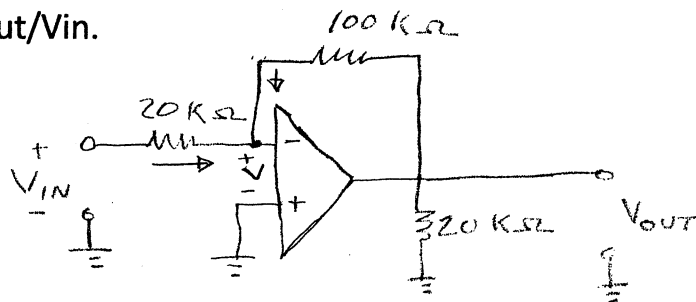3. Assuming the op amp is ideal, derive an expression for voltage gain the amplifier,  $V_{out}/V_{in}$ .



SOURCE  
HW Prob. 2,8  
p 117, textbook

$$\frac{V_{in} - V}{20K} + \frac{V_{out} - V}{100K} = 0 \quad \text{but } V=0 \text{ because ideal op Amplifier}$$



$$\frac{V_{in}}{20K} + \frac{V_{out}}{100K} = 0 \quad V=0$$

$$\frac{V_{out}}{100K} = -\frac{V_{in}}{20K} \Rightarrow \frac{V_{out}}{V_{in}} = -\frac{100K}{20K} = -5 \text{ V/V}$$

$$\boxed{\frac{V_{out}}{V_{in}} = -5 \text{ V/V}}$$

SOURCE: Example 4.2  
Textbook,  
p-181

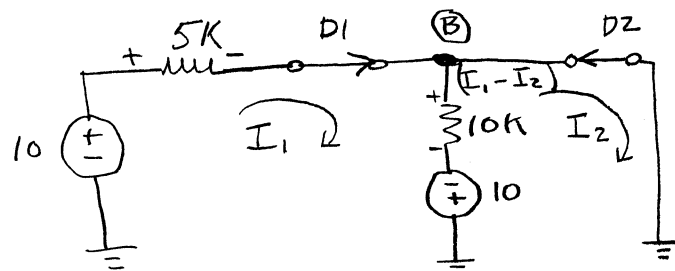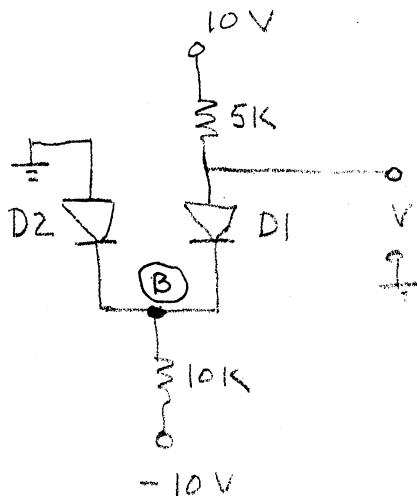4. My EE friend who graduated from Loachapoka University says both diodes in the circuit below are forward biased. Is my friend correct? No CREDIT FOR GUESSING



D1 & D2  
MARKED  
FOR FB.

$$10 - 5K I_1 - 10K (I_1 - I_2) + 10 = 0$$

$$\boxed{-15K I_1 + 10K I_2 = -20}$$

$$-10 + 10K (I_1 - I_2) = 0$$

$$-10 + 10K I_1 - 10K I_2 = 0$$


$$\boxed{10K I_1 - 10K I_2 = 10}$$

$$I_2 = \frac{\begin{vmatrix} -15K & -20 \\ 10K & 10 \end{vmatrix}}{\begin{vmatrix} -15K & 10K \\ 10K & -10K \end{vmatrix}} = \frac{-150K + 200K}{150 \times 10^6 - 100 \times 10^6} = \frac{50K}{50 \times 10^6} = 1 \mu A$$

JAYS current thru  
RB D2.

**EE is incorrect**

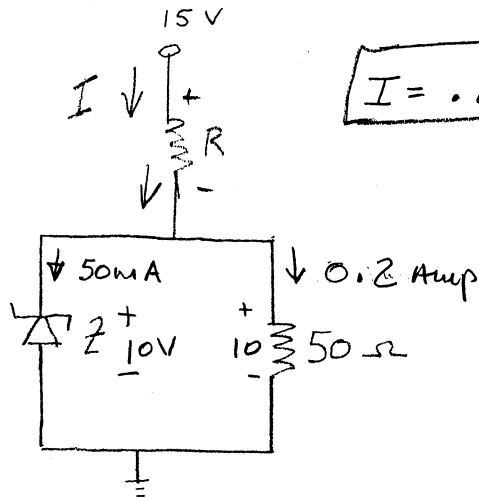5. Consider the Zener Shunt Regulator below.  $V_z = 10$  volts with  $I_z = 50$  Milliamps through the Zener. The load resistor is 50 ohms and the supply voltage is 15 volts. What is the value of  $R$ , assuming the Zener is ideal, and what is the total current supplied by the Voltage source?



$$I = .2 + 50 \text{ mA} = 250 \text{ mA}$$

$$\text{KVL} \quad 10 + R(.250) - 15 = 0$$

$$R(.250) = 5$$

$$R = 20 \Omega$$

6. A semiconductor diode normally having a forward voltage drop of 0.7 volts at 1.0 milliamp is operated at 0.5 volts. What is the resulting value of current through the diode? • BOLTZMAN'S Constant =  $1.3 \times 10^{-23}$  Joules/° Kelvin

• Charge on electron =  $1.6 \times 10^{-19}$  Coulomb

• T in degrees Kelvin  
Assume  $300^\circ \text{K}$

SOURCE  
(HW Prob. 4.19  
p. 234

$$I_D = I_S e^{V_D/V_T}$$

$$V_T = \frac{kT}{q} = \frac{1.3 \times 10^{-23} (300)}{1.6 \times 10^{-19}} = .0243 \text{ volts} \Rightarrow \text{Textbook Uses } .025 \text{ volts here}$$

$$.001 = I_S e^{.7/.0243} = I_S (3.24 \times 10^{12})$$

$$I_S = 3.086 \times 10^{-16} \text{ Amp}$$


$$\text{then } I_D = 3.086 \times 10^{-16} (e^{.5/.0243}) = 2.66 \times 10^{-7} \text{ Amp}$$

7. The operational characteristics for an nMOSFET device are shown below as well as a desired Q point for operating this device in the circuit below.

(a) from the circuit, derive the equation for the load line relating  $I_D$  and  $V_{DS}$ .

(b) What is the slope of the Load Line? <sup>DRAW IT ON THE FIGURE BELOW.</sup>  
AND

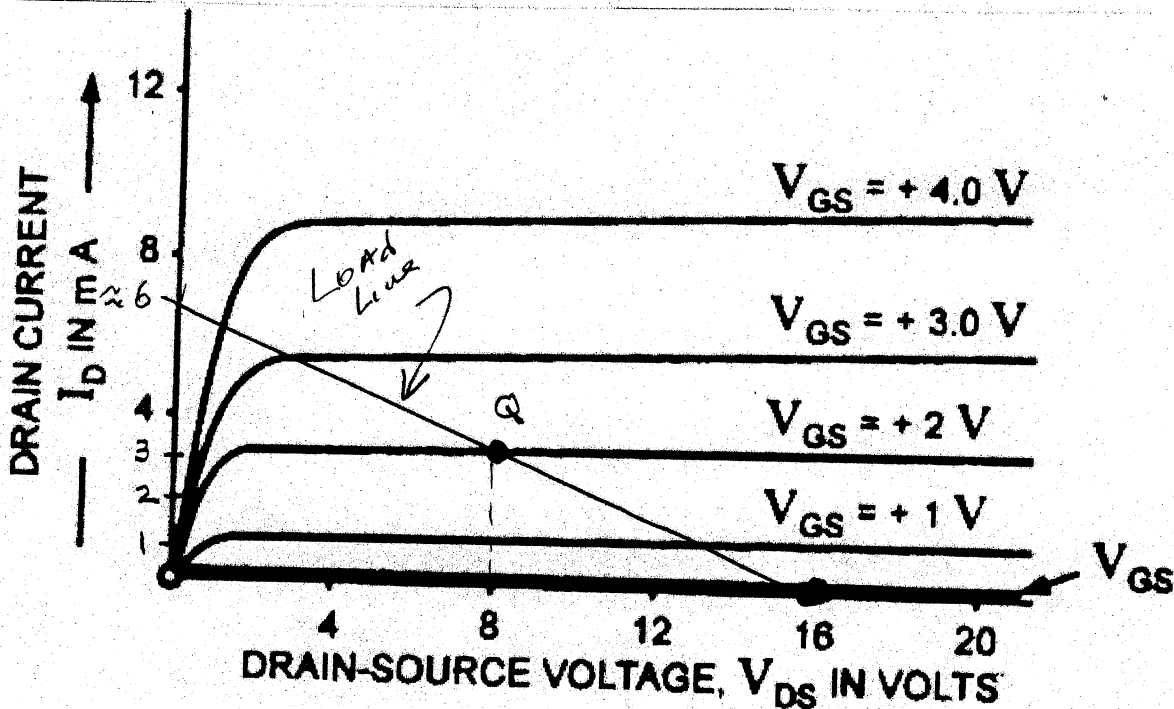(c) Compute values for resistors  $R_D$  and  $R_S$  that will "set" the device Q point as shown.



(c)

NOTE: Q point is at  $V_{GS} = 2$ ,  $V_{DS} = 8$ ,  $I_D = 3$  mA

KVL:  $-8 + R_S I_D + V_{GS} = 0$

$$-8 + R_S (.003) + 2 = 0 \Rightarrow R_S = \frac{6}{.003} = 2K$$

KVL  $-8 + R_S I_D + V_{DS} + R_D I_D - 8 = 0$  ← Load line Equation

$$-8 + 2000(.003) + 8 + R_D(.003) - 8 = 0$$

$$-8 + 6 + 8 + .003 R_D - 8 = 0$$

$$.003 R_D = 2$$

$$R_D = 2 / .003$$


$$R_D = 666.7 \Omega$$

(a)  $(R_S + R_D) I_D + V_{DS} = 16$

$$I_D = \frac{16 - V_{DS}}{R_S + R_D} = \frac{16 - V_{DS}}{2666.7}$$

When  $I_D = 0$   $V_{DS} = 16$  V

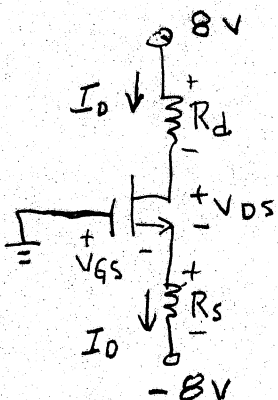(b) slope =  $\frac{1}{2666.7} = 3.75 \times 10^{-4}$



8. Given an nMOSFET device. Find Drain current,  $I_D$ , when:

Epsilon ox =  $3.45 \times 10^{-11}$  Farads/meter

$t_{ox} = 6$  nanometers

$\mu_n = 460$  cm squared/volt . sec

$V_t = 0.5$  volts

$W/L = 10$

$V_{GS} = 2.5$  volts and  $V_{DS} = 0.2$  volts

Triode Region

$$I_D = k_n' \frac{W}{L} \left[ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$k_n' = \mu_n C_{ox} = \mu_n \frac{\epsilon_{ox}}{t_{ox}} = \left[ 460 \frac{\text{cm}^2}{\text{V} \cdot \text{sec}} \right] \left[ \frac{3.45 \times 10^{-11} \frac{\text{F}}{\text{m}}}{6 \times 10^{-9} \text{m}} \right]$$

$$= \frac{460 \text{ cm}^2}{\text{volt} \cdot \text{sec}} \times 5.75 \times 10^{-3} \frac{\text{F}}{\text{m}^2} = 2.645 \frac{\text{cm}^2}{\text{m}^2} \frac{\text{Farad}}{\text{volt} \cdot \text{sec}}$$

$$= 2.645 \left[ \frac{\text{cm}^2}{1 \times 10^4 \text{ cm}^2} \right] \left[ \frac{\frac{\text{Amp} \cdot \text{sec}}{\text{volt}}}{\text{volt} \cdot \text{sec}} \right] = \underline{\underline{2.645 \times 10^{-4} \frac{\text{Amp}}{\text{V}^2}}}$$

$$I_D = 2.645 \times 10^{-4} (10) \left[ (2.5 - 0.5)(0.2) - \frac{1}{2} (0.2)^2 \right]$$

$$= 2.645 \times 10^{-3} [0.4 - 0.02]$$

$$= 2.645 \times 10^{-3} [0.38]$$

$$\boxed{I_D = 1 \text{ mA}}$$

SOURCE  
HW Problem 5.14(c)

First Test Region of  
operation.

$$V_{DS} \geq V_{GS} - V_t \text{ in Sat.}$$






$$0.2 \geq 2.5 - 0.5$$

$$0.2 \geq 2$$

No - Triode  
Region

9. (a) Which are pMOSFETS and which are nMOSFET devices?

(b) what is the region of operation ( triode, saturation, or boundary for each device given the data shown?

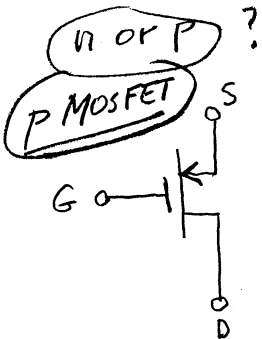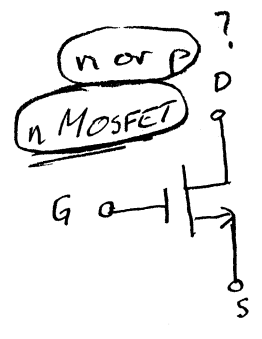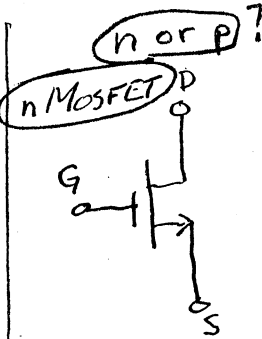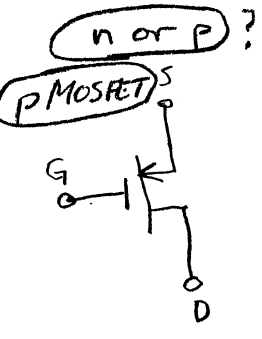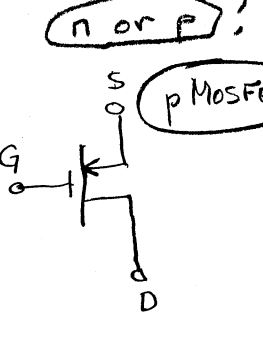 <p>n or p ? p MOSFET</p>	 <p>n or p ? n MOSFET</p>	 <p>n or p ? n MOSFET</p>	 <p>n or p ? p MOSFET</p>	 <p>n or p ? p MOSFET</p>
$V_{ov} = 2 \text{ volts}$ $V_{SD} = 4 \text{ volts}$ $V_{SD} \geq V_{ov}$	$V_{ov} = 3 \text{ volts}$ $V_{DS} = 3.5 \text{ volts}$ $V_{DS} \geq V_{ov}$ yes	$V_{GS} = 2 \text{ volts}$ $V_{tn} = 0.5 \text{ volts}$ $V_{DS} = 1 \text{ volt}$ $V_{DS} \geq V_{ov}$ <u>No</u>	$V_{ov} = 2 \text{ volts}$ $V_{SD} = 1.5 \text{ volts}$ $V_{SD} \geq V_{ov}$ <u>No</u>	$V_{ov} = 2 \text{ volts}$ $V_{SD} = 2 \text{ volts}$ $V_{SD} \geq V_{ov}$ = Boundary
REGION? SATURATION	REGION? SATURATION	REGION? Triode	REGION? Triode	REGION? Boundary Region

10. Given an nMOSFET device where:

$k_n(\text{primed}) = 400 \text{ microamps/Volt (squared)}$

Threshold voltage = 0.5 volts

$V_{gs} = V_{ds} = V_{supply} = 1.8 \text{ volts}$

Drain current  $I_d = 2 \text{ milliamps}$

$L = 0.18 \text{ micrometers}$

Source

HW Problem 5.20,  
page 295

FIND W

Determine Region of Operation: Is  $V_{ds} \geq V_{gs} - V_t$   
 $1.8 \geq 1.8 - 0.5$   
yes SATURATION

$$I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2$$

$$.002 = \frac{1}{2} \left[ 400 \times 10^{-6} \frac{\text{Amps}}{\text{V}^2} \right] \left[ \frac{W}{.18 \times 10^{-6}} \right] [1.8 - .5]^2 \text{ V}^2$$

$$.002 = \frac{200 \times 10^{-6}}{.18 \times 10^{-6}} (1.3)^2 W$$

$$.002 = 1877.77 W$$

$$W = 1.065 \mu\text{m}$$