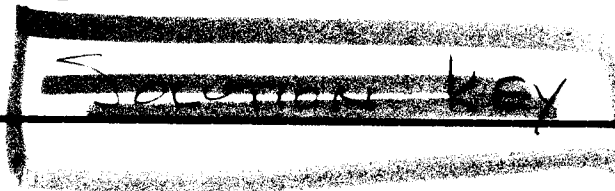


# Test 1

**EE315 Spring 2017—Dr. B**

**NAME** \_\_\_\_\_



**DO ALL YOUR WORK ON THIS EXAM.  
USE THE BACK SIDES of EXAM PAPER IF  
NECESSARY BUT POINT ME WHERE YOU  
DID THAT.**

- ***Your Equation sheet must be turned in with the Exam.***
- ***NO Cell PHONE Calculators allowed. Other calculators ok.***
- ***Closed books/closed lecture notes.***
- ***Each Problem worth 18 points.***


"Engineers like to solve problems. If there are no problems handily available, they will create their own problems."

— Scott Adams

**Problem 1: Circle either true or false (1 point each):**

1. (True **False**) Amplifier power gain is  $20 \log V_{out}/V_{in}$ .
2. (True **False**) Amplifier "efficiency" is defined as how accurately the output signal "follows" the input signal.
3. (True **False**) The ideal operational amplifier has the following characteristics: infinite output resistance, zero input resistance, finite gain, and infinite bandwidth.
4. (**True** False) The operational amplifier "rail voltages" providing DC power to the amplifier provide saturation limits for the amplitudes of the amplifier's output voltage.
5. (**True** False) An ideal operational amplifier has zero common mode gain, or said another way, infinite common mode rejection.
6. (**True** False) A good example of a common mode signal is noise.
7. (True **False**) There are two types of input terminals for the operational amplifier; the inverting and the difference input.
8. (True **False**) Voltage gain in decibels is  $10 \log (V_{out}/V_{in})$ .
9. (**True** False) A Voltage Follower is a unity gain amplifier.
10. (**True** False) Negative feedback is applied to an operational amplifier to control the amount of gain the amplifier will provide.

2.

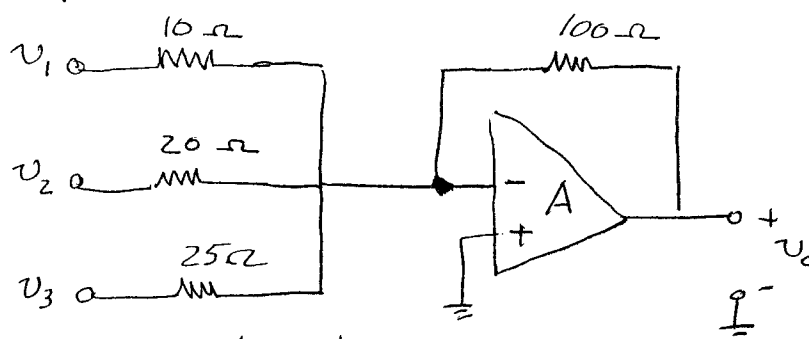


Given  $A \rightarrow \infty$   
 $R_{in} \rightarrow \infty$   
 $R_o \rightarrow 0$

Write the equation for  $v_0$  as a function of  $v_1, v_2, v_3$ .

$$v_0 = - \left[ \frac{100}{10} v_1 + \frac{100}{20} v_2 + \frac{100}{25} v_3 \right]$$

$$v_0 = -10v_1 - 5v_2 - 4v_3$$

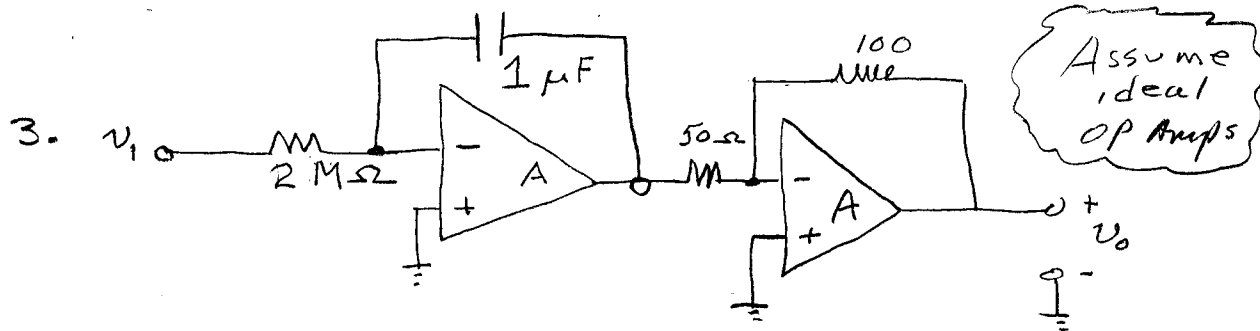

Find Expression for  $v_o(t)$ .

$$v_o = -\frac{100}{50} \left[ -\frac{1}{(2M)(1\mu F)} \int v_i dt \right]$$

$$= \frac{2}{2} \int v_i dt = \boxed{\int v_i dt = v_o}$$

4. Given  $v(t) = 10 \sin \omega t$  volts

$i(t) = 40 \sin \omega t$  amps


(a) Express  $v(t)$  in RMS value

(b) Express  $i(t)$  in RMS value

$$(a) .707(10) = 7.07 \text{ volts}$$

$$(b) .707(40) = 28.28 \text{ Amps}$$

5. Given

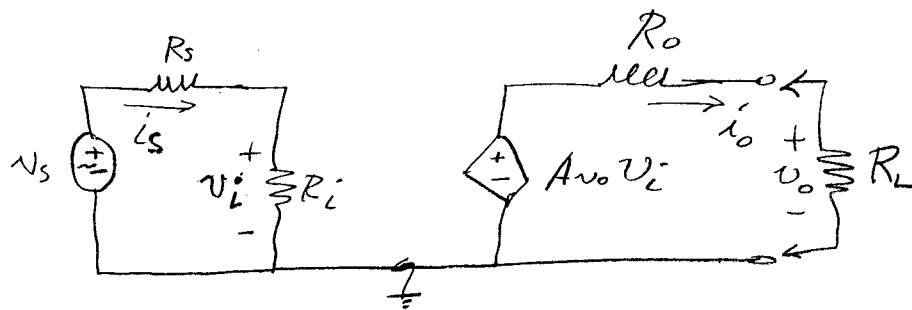

Find Equations for  $A_v = \frac{v_o}{v_s}$  and  $A_i = \frac{i_o}{i_s}$

Given  $A_{vo} = 100 \text{ V/V}$

$$v_o = \left( \frac{R_L}{R_o + R_L} \right) A_{vo} v_i \quad v_i = \left( \frac{R_i}{R_s + R_i} \right) v_s$$

$$v_o = \left( \frac{R_L}{R_o + R_L} \right) A_{vo} \left( \frac{R_i}{R_s + R_i} \right) v_s$$

$$\frac{v_o}{v_s} = \frac{(R_L R_i) A_{vo}}{(R_o + R_L)(R_s + R_i)} = \frac{100 R_L R_i}{(R_o + R_L)(R_s + R_i)}$$



$$i_o = \left( \frac{A_{vo} v_i}{R_o + R_L} \right) = \frac{100 v_i}{R_o + R_L} \text{ and } v_i = i_s R_i$$

$$i_o = \left( \frac{100}{R_o + R_L} \right) (R_i) i_s$$

$$\frac{i_o}{i_s} = \frac{100 R_i}{R_o + R_L}$$

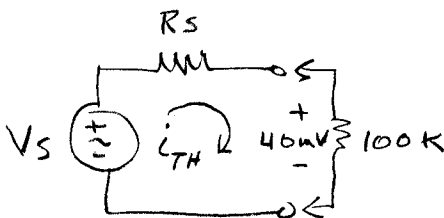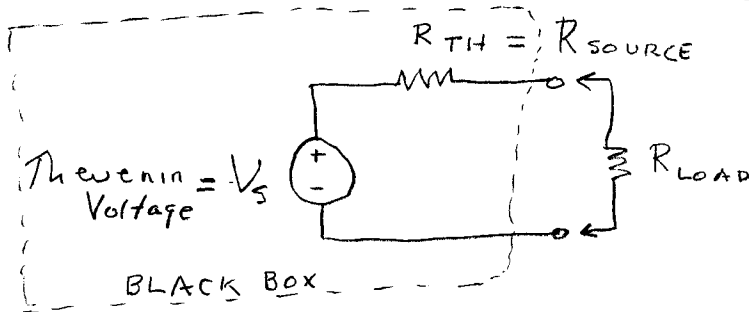
6. An unknown signal source produces a voltage across a 100 K ohm load resistor of 40 millivolts (data point 1) and 10 millivolts across a load resistor of 10 K ohm (data point 2).

Your task: from the experimental data above, what is the Thevenin voltage, the Norton current, and the internal resistance of the signal source?



$$V_o = \left( \frac{100 \text{ K}}{R_s + 100 \text{ K}} \right) V_s = 40 \text{ mV}$$
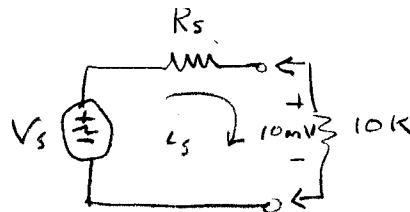
$$\text{OR } V_s = \frac{(40 \text{ mV})(R_s + 100 \text{ K})}{100 \text{ K}}$$



$$V_o = \left( \frac{10 \text{ K}}{R_s + 10 \text{ K}} \right) V_s = 10 \text{ mV}$$

$$V_s = \frac{10 \text{ mV} (R_s + 10 \text{ K})}{10 \text{ K}}$$

$$\text{Then } \frac{40 \text{ mV} (R_s + 100 \text{ K})}{100 \text{ K}} = \frac{10 \text{ mV} (R_s + 10 \text{ K})}{10 \text{ K}}$$

$$1000 (R_s + 10 \text{ K}) = 400 (R_s + 100 \text{ K})$$

$$1000 R_s + 1 \times 10^7 = 400 R_s + 4 \times 10^7$$

$$600 R_s = 3 \times 10^7$$

$$R_s = 50 \times 10^4 = 50 \text{ K} \Omega = R_{TH}$$

$$\text{Then } V_s = V_{TH} \Rightarrow \frac{40 \text{ mV} (50 \times 10^3 + 100 \times 10^3)}{100 \text{ K}} = .06 \text{ Volts}$$

$$V_{TH} = 60 \text{ mV}$$

$$I_{SC} = \frac{V_{TH}}{R_{TH}} = \frac{60 \text{ mV}}{50 \text{ K}} = 1.2 \mu \text{ A}$$