

Test 2 MAKE-UP

EE315 Spring 2017—Dr. B

NAME Solution Key

**DO ALL YOUR WORK ON THIS EXAM.
USE THE BACK SIDES of EXAM PAPER IF
NECESSARY BUT POINT ME WHERE YOU
DID THAT.**

- ***Your Equation sheet must be turned in with the Exam.***
- ***NO Cell PHONE Calculators allowed. Other calculators ok.***
- ***Closed books/closed lecture notes.***
- ***Each Problem worth 18 points.***

○ *A good engineer is someone who is good with math but without the personality of an accountant,*

EE315 SPRING TERM 2017

TEST 2 MAKEUP- 29 MARCH 2017

NAME


Solution Key

CIRCLE TRUE OR FALSE (1 point each)

1. (T/~~F~~) Thermal voltage for a semiconductor diode depends on temperature (in Centigrade degrees), Boltzmann's Constant, and charge on the electron. ^{Kelvin}
2. (T/~~F~~) An extrinsic semiconductor does not have any doping to change the conductivity of the material. ^{intrinsic}
3. (T/~~F~~) A semiconductor diode has only two states; either forward biased or electrically biased. ^{reversed}
4. (~~T~~/F) At room temperature, thermal voltage for silicon is 25 microvolts.
5. (~~T~~/F) A depletion region in a semiconductor diode is a region free of charge carriers.
6. (~~T~~/F) A semiconductor diode is formed by a p-n junction.
7. (~~T~~/F) A Zener diode must be reversed biased to perform and operate as a Zener diode.
8. (~~T~~/F) A "hole" is the empty space where an electron was but the space still has an effective mass and electrical charge.
9. (T/~~F~~) A reversed biased semiconductor diode is, ideally, a ^{open} short circuit.
10. (T/~~F~~) An "n region" in a semiconductor diode is a region where an excess of positive charges are available for conduction. ^{negative}

2. A newly hired EE recently graduated from Loachapoka University School of Engineering tells you that both diodes in circuit below are forward biased. Is the EE correct? YES or NO?

Show your work!! NO CREDIT FOR GUESSING

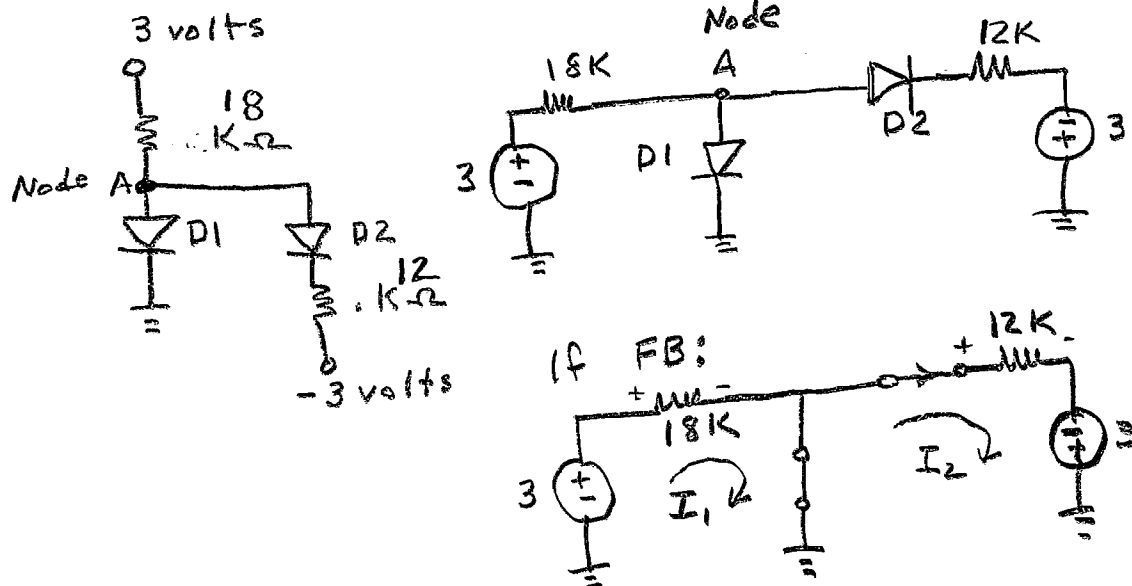

$$3 - 18K I_1 = 0$$

$$I_1 = 3/18K = 1.67 \times 10^{-4} \text{ Amp}$$

$$-12K I_2 + 3 = 0$$

$$I_2 = 3/12K = 2.5 \times 10^{-4} \text{ Amp}$$

For D_1

$$I_{D1} = I_1 - I_2 = 1.67 \times 10^{-4} - 2.5 \times 10^{-4}$$

$$= -0.83 \times 10^{-4}$$

Since I_{D1} is negative direction,
 D_1 cannot be forward biased.

Engineer is incorrect!

3. A step down transformer has the following data:


$V_p = 120$ volts ac at 60 hz

$N_p = 400$

$N_s = 200$

$Z_s = 10$ ohm

FIND V_s , I_s , and I_p

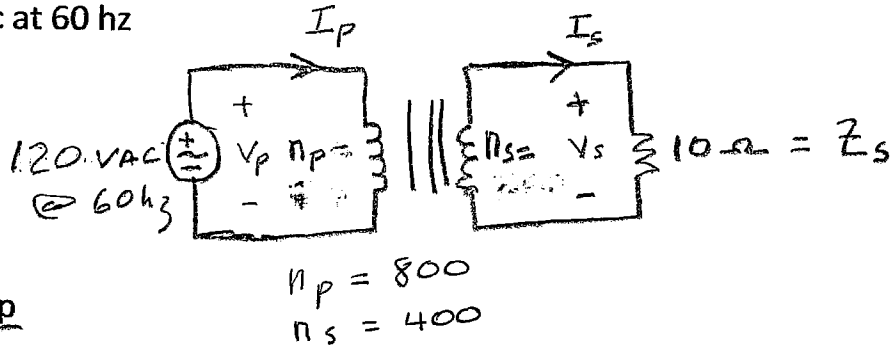

Recall $\frac{N_p}{N_s} = \frac{V_p}{V_s} = \frac{I_s}{I_p}$

Then $\frac{800}{400} = \frac{120}{V_s} \Rightarrow V_s = 60 \text{ volts}$

Then $I_s = \frac{V_s}{10} = \frac{60}{10} = 6 \text{ Amps}$

Then $\frac{N_p}{N_s} = \frac{I_s}{I_p} \Rightarrow I_p = \frac{N_s I_s}{N_p} = \frac{400}{800} (6)$

$I_p = 3 \text{ Amps}$

4. A diode operating in forward bias has a voltage drop of 0.7 volts at 1.2 mA. The diode is then operated at 0.5 milliamp. What is the new value of diode voltage? Assume $V_T = 25$ millivolts.

$$I_D = I_S (e^{V_D/V_T} - 1)$$

$$1.2 \times 10^{-3} = I_S (e^{0.7/0.025} - 1) = I_S e^{28}$$

$$I_S = \frac{1.2 \times 10^{-3}}{1.4462 \times 10^{12}} = 8.297 \times 10^{-16} \text{ Amp}$$

$$\text{then } I_D|_{0.5 \text{ mA}} = 8.297 \times 10^{-16} (e^{V_D/0.025} - 1)$$

$$0.0005 = 8.297 \times 10^{-16} e^{V_D/0.025}$$

$$6.026 \times 10^{11} = e^{V_D/0.025}$$


$$27.124 = V_D / 0.025$$

$$\boxed{V_D = 0.678 \text{ volts}}$$

5. A Zener shunt regulator is shown below. Datasheet for the Zener shows:

$V_z = 6.0$ volts at $I_z = 5$ milliamp and $r_z = 10$ ohm.

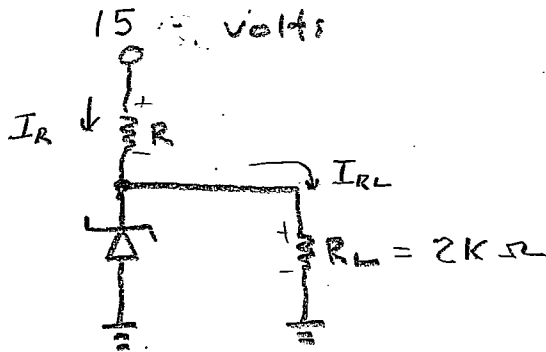- (a) Find V_{z0} for the Zener diode
 (b) Find the current through R_L at that Zener voltage
 (c) Find the current through R
 (d) Find value for R



$$(a) V_z = V_{z0} + r_z I_z$$

$$V_{z0} = V_z - r_z I_z$$

$$= 6 - 10(.005)$$

$$V_{z0} = 5.95 \text{ volts}$$

$$(b) I_{RL} = \frac{6}{2k} = 3 \text{ mA}$$

$$R_L I_{RL} + R I_R - 15 = 0$$

$$I_{RL} = 3 \text{ mA}$$

$$(c) \text{ so } I_R = 3 \text{ mA} + 5 \text{ mA} = 8 \text{ mA}$$


$$(d) \text{ so } 2k(.003) + R(.008) - 15 = 0$$

$$6 + .008R - 15 = 0$$

$$.008R = 9$$

$$R = 1125 \Omega$$

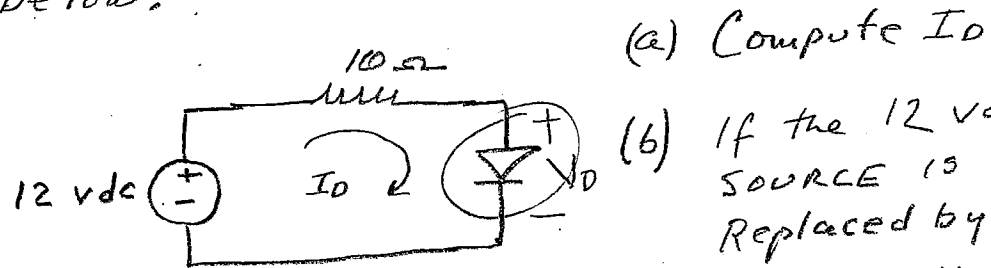6. Using the Constant Voltage Drop Model for a Semiconductor Diode in the circuit below:



(b) If the 12 VDC SOURCE IS Replaced by a 12 V peak sinusoid waveform, sketch V_D waveform.

