

Electric Circuits & Electronics
Design Lab EE 316-03
Lab 1: Circuits Review

By: Austin Brown

Introduction:

The purpose of this lab is to review essential concepts such as Ohm's Law, Kirchhoff's Current and voltage laws. We will also familiarize ourselves with the Multisim simulation software. The first section of this report is dedicated to hand calculations. The next section is dedicated to simulating the circuits. Then I will discuss the results.

Theoretical Analysis:

The first part of the lab is to calculate the branch voltages, mesh currents, node voltages, and loop currents of figure 1.3. First this will be done by using the exact values, then with the resistors being 10% above the exact value, and then with the resistors being 10% below their exact value. The circuit and values are shown below.

$$V_s = 5.0V$$

$$R_1 = R_2 = R_3 = 100$$

$$R_4 = R_5 = 1\text{ K}$$

$$R_6 = R_7 = 2.2\text{ K}$$

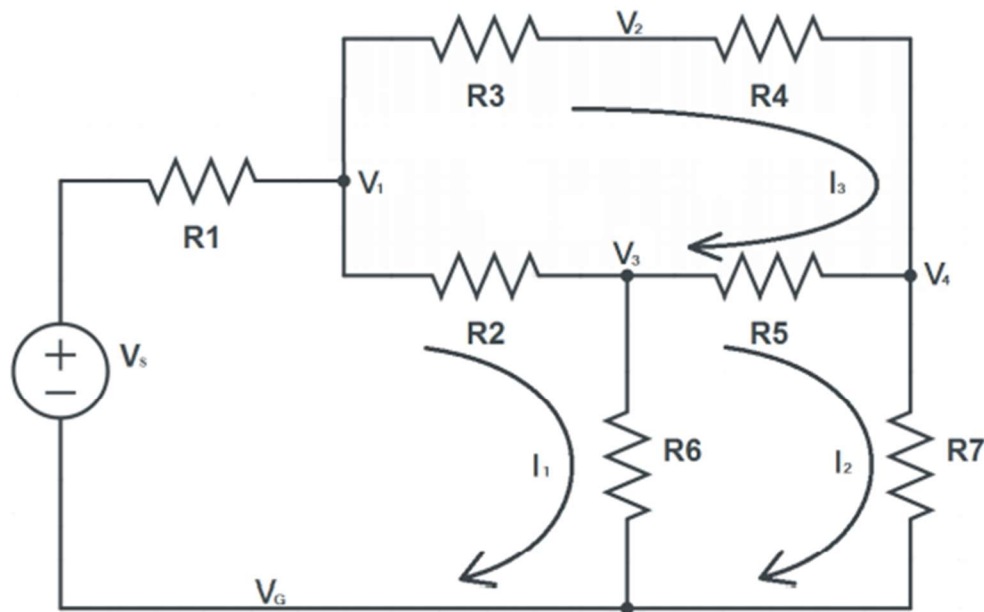


Figure 1.3

Hand Computation: Exact Values

Branch Node or Loop Number	Branch Voltage(V)	Branch Currents(mA)	Node Voltages(V)	Loop Currents(mA)	
1	.363	3.364	4.637	3.654	
2	0.272	2.719	4.545	1.650	
3	0.092	0.915	4.365	.916	
4	0.915	0.915	3.630		
5	0.735	.735			
6	4.365	1.984			
7	3.630	1.650			


Hand Computation: 10% Above Exact

Branch Node or Loop Number	Branch Voltage(V)	Branch Currents(mA)	Node Voltages(V)	Loop Currents(mA)	
1	.363	4.038	4.637	4.038	
2	0.272	3.021	4.545	1.833	
3	0.090	1.017	4.365	1.017	
4	0.915	1.017	3.630		
5	0.735	0.816			
6	4.365	2.205			
7	3.629	1.833			

Hand Computation: 10% Below Exact

Branch Node or Loop Number	Branch Voltage(V)	Branch Currents(mA)	Node Voltages(V)	Loop Currents(mA)	
1	0.363	3.304	4.637	3.304	
2	0.272	2.472	4.545	1.500	
3	0.092	0.832	4.365	0.832	
4	0.915	0.832	3.630		
5	0.735	0.668			
6	4.366	1.804			
7	3.630	1.500			

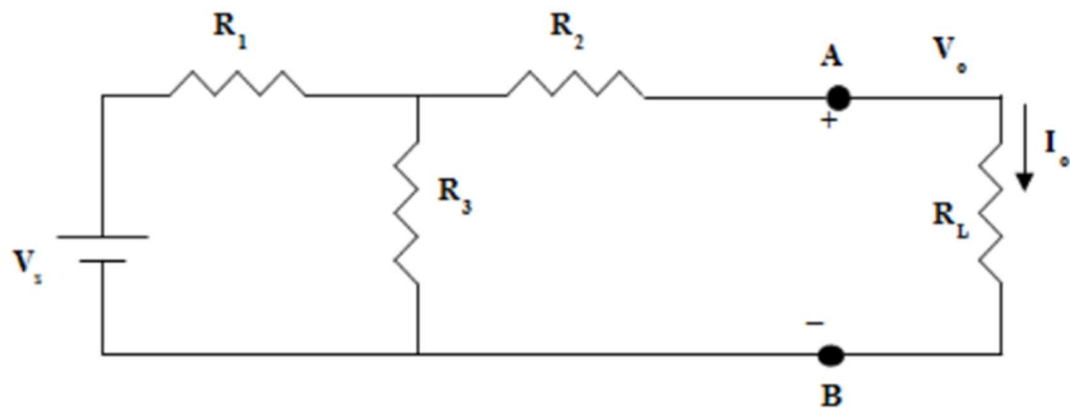
The next task is to analyze figure 1.4 to determine its Norton and Thevenin equivalent circuits. The work is shown in the appendix.




Simulations:

In this part of the lab, we use Multisim to simulate the circuits that we just analyzed by hand. I first simulated the circuit from figure 1.

Simulation of exact voltage values

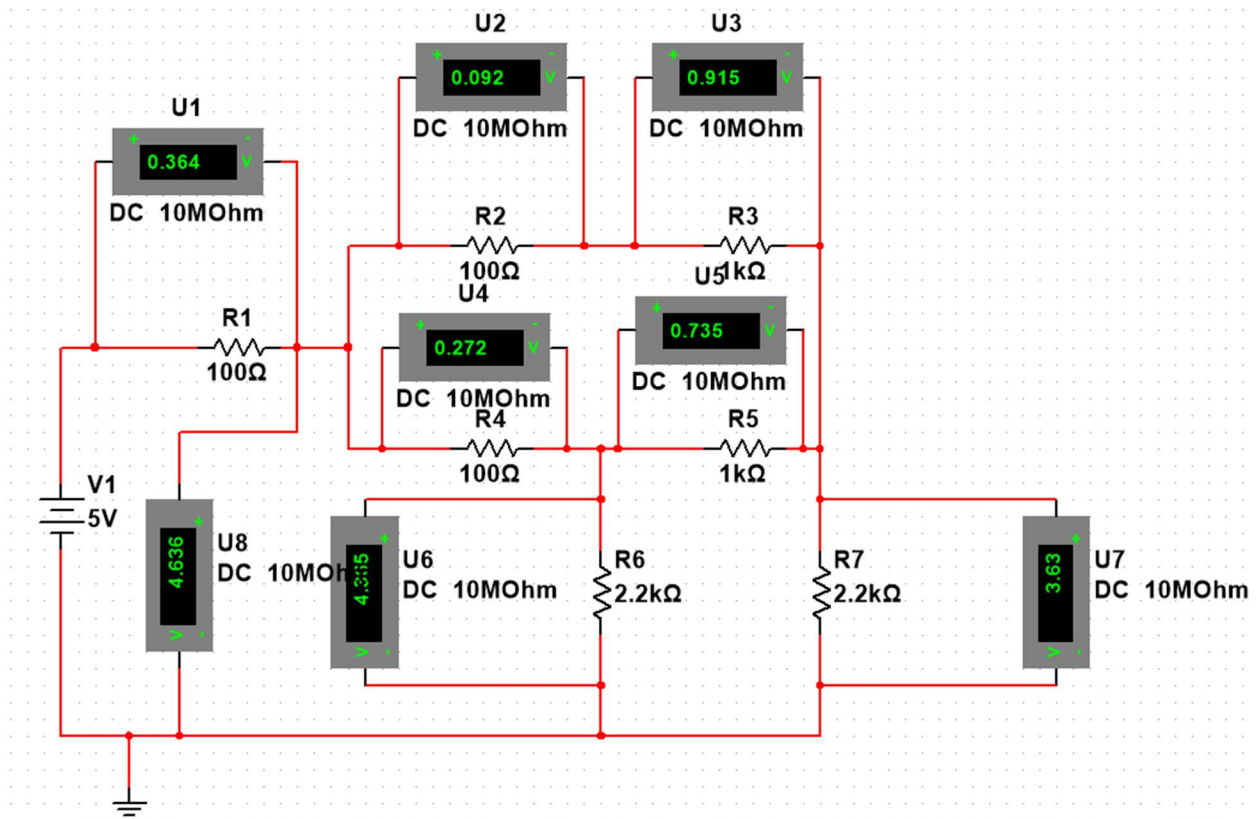

Simulation of exact current readings.

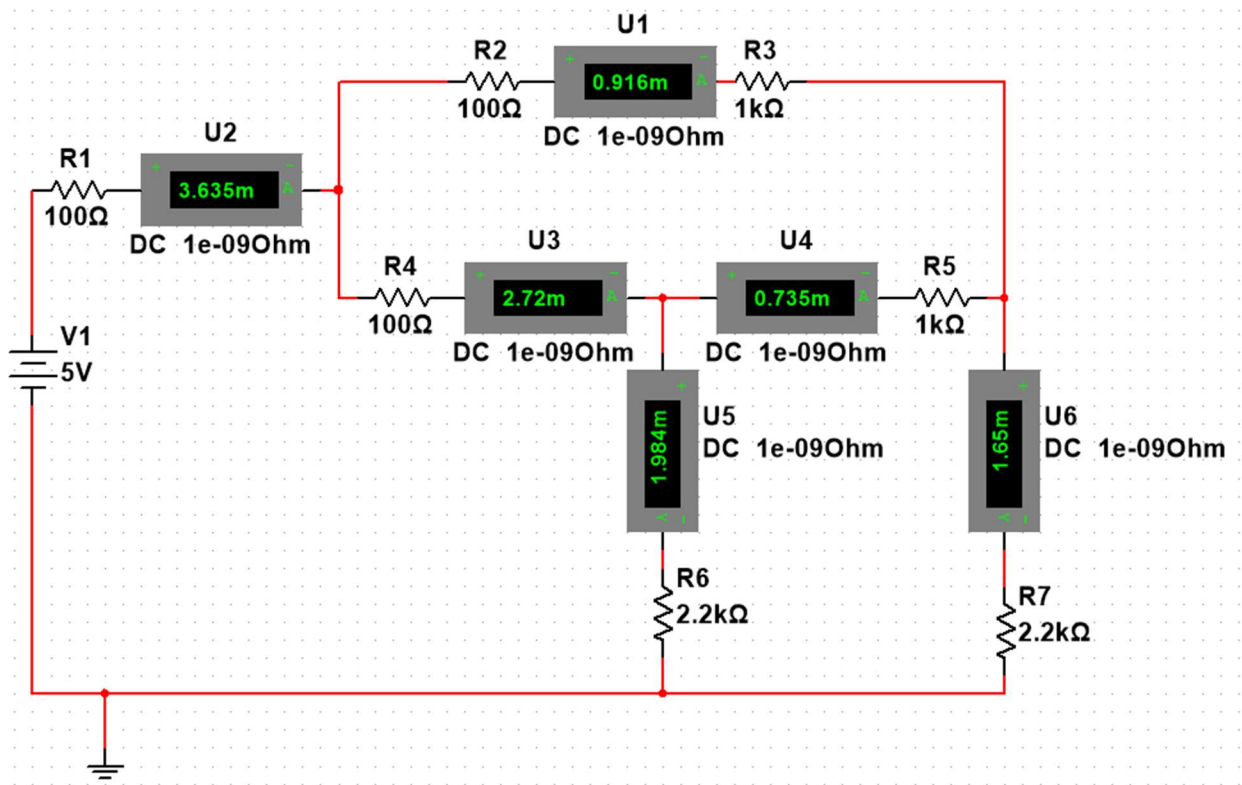

Exact Values

Branch Node or Loop Number	Branch Voltage(V)	Branch Currents(mA)	Node Voltages(V)	Loop Currents(mA)
1	.364	3.365	4.637	3.655
2	0.272	2.72	4.545	1.65
3	0.092	0.916	4.365	.916
4	0.915	0.916	3.63	
5	0.735	.735		
6	4.365	1.984		
7	3.63	1.65		


10% above exact values

Branch Node or Loop Number	Branch Voltage(V)	Branch Currents(mA)	Node Voltages(V)	Loop Currents(mA)
1	.363	4.039	4.637	4.039
2	0.272	3.021	4.547	1.833
3	0.090	1.017	4.365	1.017
4	0.915	1.017	3.63	
5	0.735	0.817		
6	4.365	2.204		
7	3.630	1.833		


10% below exact values

Branch Node or Loop Number	Branch Voltage(V)	Branch Currents(mA)	Node Voltages(V)	Loop Currents(mA)
1	.363	3.303	4.637	3.303
2	0.272	2.472	4.544	1.500
3	0.090	0.832	4.365	0.832
4	0.915	0.832	3.63	
5	0.735	0.669		
6	4.365	1.804		
7	3.630	1.500		



Below is the Open Circuit Voltage.

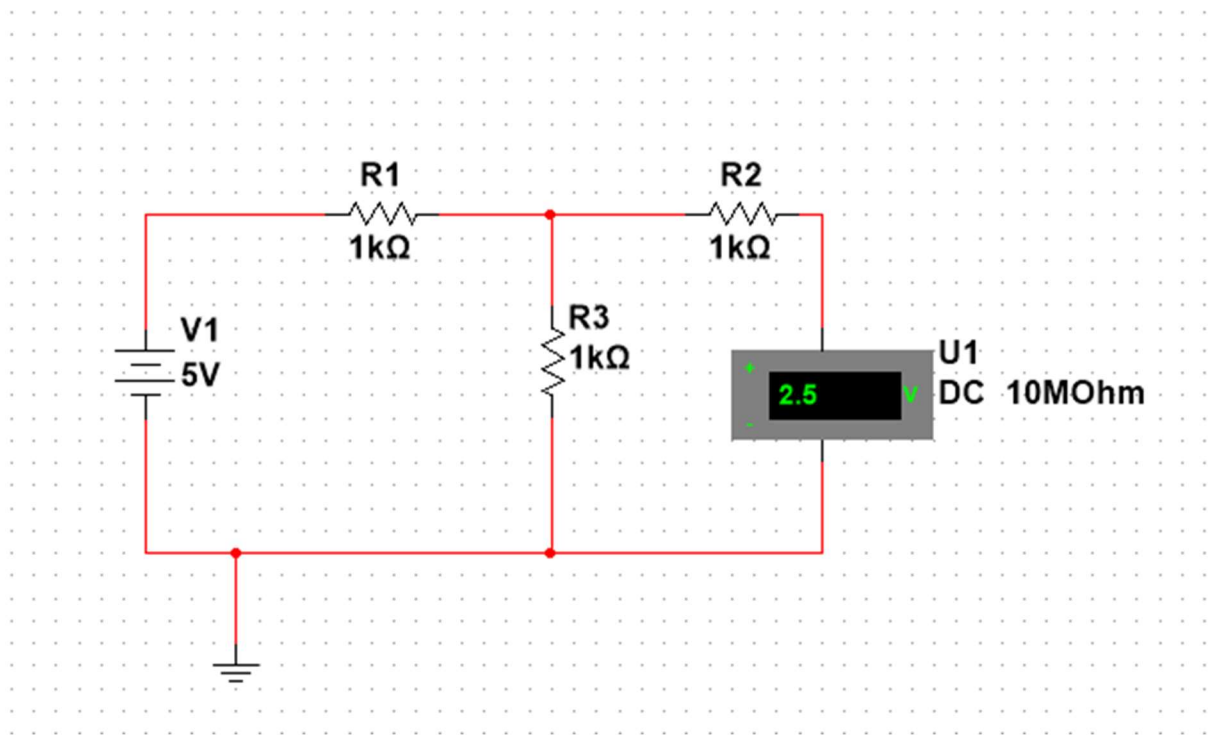

Below is the short circuit current.

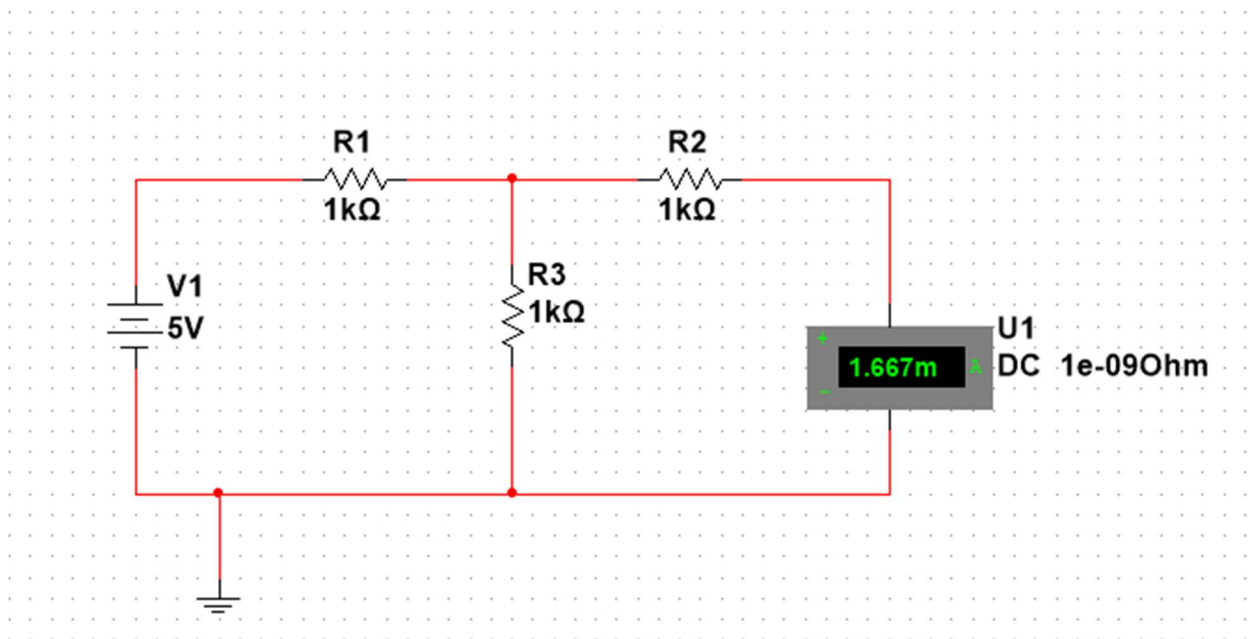

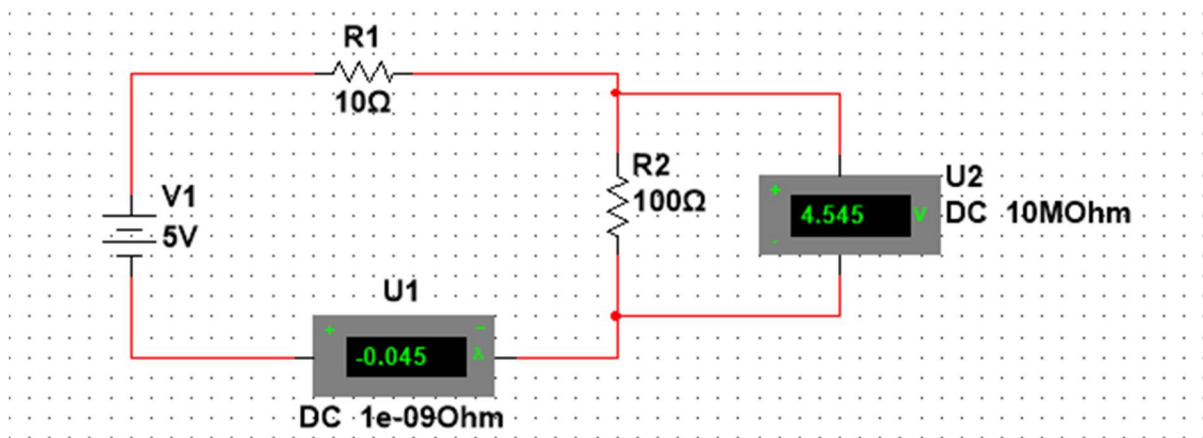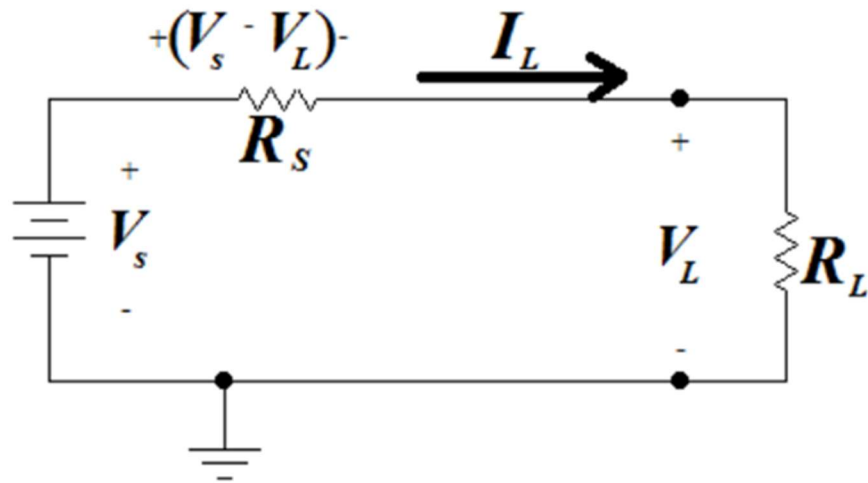The next task is to set V_s to 5 volts and R_s to 100 Ohms. We will change R_L from 10 Ohms to 1k Ohms.



$R_L (\Omega)$	$V_L (V)$	$I_L (A)$
10	0.455	0.045
20	0.833	0.042
40	1.429	0.036
70	2.059	0.029
100	2.500	0.025
150	3.000	0.020
200	3.333	0.017
300	3.750	0.013
500	4.167	0.005
1000	4.545	0.005

Results and Discussion:

In this lab, we analyze several circuits by hand and then simulate them. The purpose of this is to determine if simulation is a valid way of testing and validating a circuit. The hand computations and simulations. The hand computations and simulations closely match each other.


Branch Node or Loop Number	Branch Voltage(V)	Branch Currents(mA)	Node Voltages(V)	Loop Currents(mA)	
1	.363	3.364	4.637	3.654	
2	0.272	2.719	4.545	1.650	
3	0.092	0.915	4.365	.916	
4	0.915	0.915	3.630		
5	0.735	.735			
6	4.365	1.984			
7	3.630	1.650			

Branch Node or Loop Number	Branch Voltage(V)	Branch Currents(mA)	Node Voltages(V)	Loop Currents(mA)
1	.364	3.365	4.637	3.655
2	0.272	2.72	4.545	1.65
3	0.092	0.916	4.365	.916
4	0.915	0.916	3.63	
5	0.735	.735		
6	4.365	1.984		
7	3.63	1.65		

The results of this lab also validate Ohm's law, Kirchhoff's voltage and currents laws, and Thevenin and Norton circuits. The experiment where we change the resistor value confirms Ohm's law.

$R_L (\Omega)$	$V_L (V)$	$I_L (mA)$
10	0.455	0.045
20	0.833	0.042
40	1.429	0.036
70	2.059	0.029
100	2.500	0.025


150	3.000	0.020
200	3.333	0.017
300	3.750	0.013
500	4.167	0.005
1000	4.545	0.005

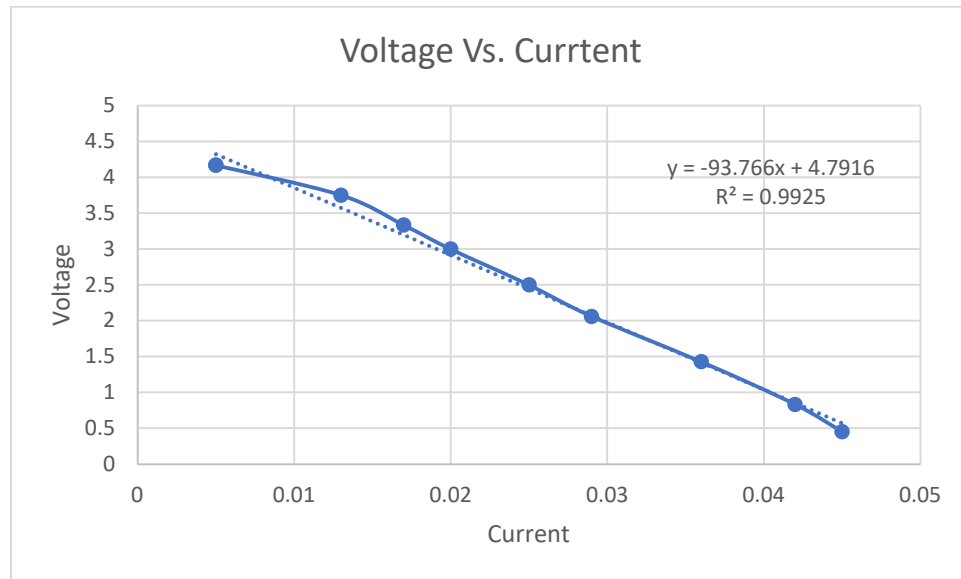

Conclusion:

The purpose of this lab was to verify some fundamental circuit theory. There was almost no difference between the hand computations and the simulations. We also gained experience using the Multisim software.

Appendix

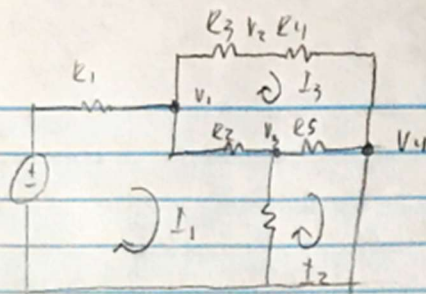

$$V_s = 5.0 \text{ V}$$

$$R_1 = R_2 = R_3 = 100$$

$$R_4 = R_5 = 1k$$

$$R_6 = R_7 = 2.2k$$

loop 1: $5 - 100I_1 - 100(I_1 - I_3) - 2200(I_1 - I_2) = 0$
 $5 - 100I_1 - 100I_1 - 2200I_1 + 100I_3$
 $5 = 2400I_1 - 2200I_2 + 100I_3$


loop 2: $-2200(I_2 - I_1) - 1000(I_2 - I_3) - 2200I_2 = 0$
 $2200I_1 - 5400I_2 + 1000I_3 = 0$

loop 3: $-100I_3 - 1000I_3 - 1000(I_3 - I_2) - 100(I_3 - I_1) = 0$
 $100I_1 + 1000I_2 - 2200I_3 = 0$

$$\begin{bmatrix} 2400 & -2200 & 100 \\ 2200 & -5400 & 1000 \\ 100 & 1000 & -2200 \end{bmatrix} \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix} \begin{matrix} I_1 = .00367 \text{ A} \\ I_2 = .00165 \text{ A} \\ I_3 = .00092 \text{ A} \end{matrix}$$

$$\begin{bmatrix} 2640 & -2420 & -110 \\ -2420 & -5440 & 1100 \\ 110 & 1100 & -2420 \end{bmatrix} \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix} \begin{matrix} I_1 = .0033 \text{ A} \\ I_2 = .00165 \text{ A} \\ I_3 = .00083 \text{ A} \end{matrix}$$
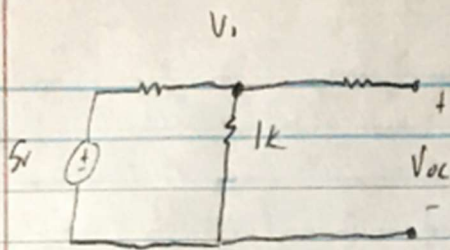
$$\begin{bmatrix} 2160 & -1980 & -90 \\ 1980 & -4860 & 900 \\ 90 & 900 & -1980 \end{bmatrix} \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix} \begin{matrix} I_1 = .0044 \text{ A} \\ I_2 = .00183 \text{ A} \\ I_3 = .00108 \text{ A} \end{matrix}$$




$$\frac{V_1 - 5}{1k} + \frac{V_1}{1k} = 0$$

$$V_1 = V_{oc} = 2.5$$

$$V_1 - 5 + V_1 = 0$$

$$V_1 = 5/2 \text{ V}$$

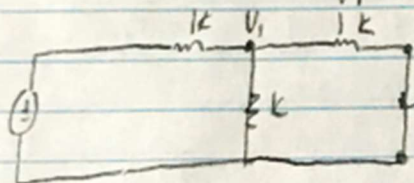


$$\frac{V_1 - 5}{1k} + \frac{V_1}{1k} + \frac{V_1}{1k} = 0$$

$$V_1 - 5 + V_1 + V_1 = 0$$

$$3V_1 = 5$$

$$V_1 = 1.66 \text{ V}$$

Thevenin

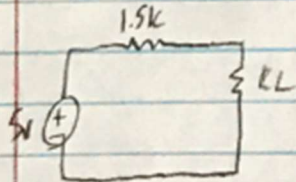

Norton

