
## **Austin Brown**

## Prelab 4

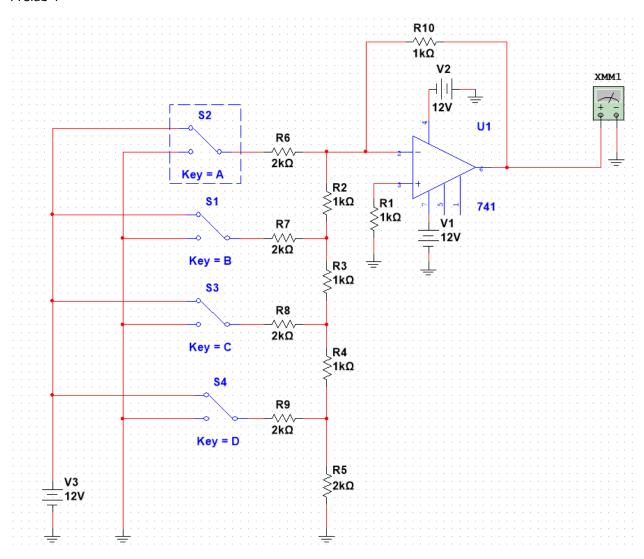

Input State					Simulation
	V <sub>A</sub>	V <sub>B</sub>	Vc	V <sub>D</sub>	V <sub>o</sub> (V)
0	0	0	0	0	0.002
1	0	0	0	1	-0.310
2	0	0	1	0	-0.623
3	0	0	1	1	-0.935
4	0	1	0	0	-1.248
5	0	1	0	1	-1.56
6	0	1	1	0	-1.975
7	0	1	1	1	-2.185
8	1	0	0	0	-2.498
9	1	0	0	1	-2.81
10	1	0	1	0	-3.123
11	1	0	1	1	-3.435
12	1	1	0	0	-3.748
13	1	1	0	1	-4.06
14	1	1	1	0	-4.373
15	1	1	1	1	-4.685